

CMPE 160 Laboratory Exercise 06
Binary Addition and Subtraction Circuits

Christopher Larson
Performed: 21 February 2018
Submitted: 28 February 2018

Lab Section: L3
Instructor: Mr. Dominguez
TA: Andrew Ramsey
Matthew Millar
Madeline Mooney

Lecture Section: 01
Professor: Professor Beato

By submitting this report, you attest that you neither have given nor have received any assistance (including writing, collecting data, plotting figures, tables or graphs, or using previous student reports as a reference), and you further acknowledge that giving or receiving such assistance will result in a failing grade for this course.

Your Signature: _____

Abstract

The objective of this exercise was to design, and implement binary arithmetic circuits, such as a one-bit full adder and a four-bit full adder/subtractor. The full adder was designed and constructed using basic logic gates, and the four-bit full adder/subtractor was built using a four-bit full adder chip. Full-adders perform addition between two binary numbers and accounts for values carried in as well as out. For a one-bit adder there are three inputs, A, B and Carry-In and two outputs, the Sum and the Carryout. The four-bit adder takes in four inputs and returns five outputs, and uses two's-complement to represent negative numbers. The one-bit adder was expressed as a boolean expression and simplified using a Karnaugh map, which was used to build a schematic diagram of the circuit. The schematic was used to simulate the waveforms of the one-bit adder to confirm the correct of the circuit by comparing it against a test bench, the waveforms and design of the circuit were shown to be correct. Once the design was found to be correct the schematic was transferred onto a breadboard and tested for correctness, which it was found to be. A four-bit adder/subtractor was also designed and transferred onto a breadboard, which was tested for correctness by comparing the results to hand-computed results. The four-bit adder/subtractor was found to be correctly designed as the tested results matched the expected results.

Design Methodology

The boolean expression used to create the sum of products expressions was $Sum = \Sigma_{ABCin}(1, 2, 4, 7)$ and $Carryout = \Sigma_{ABCin}(3, 5, 6, 7)$. The Karnaugh map representations of the expressions are shown in Figure 1 for the Sum and Figure 2 for the CarryOut.

		$BCin$			
		00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0

Figure 1: K-map of Sum

The equation given from the K-map in Figure 1 is shown in Equation 1. This expression was further simplified by changing the AND and OR gates to XOR, shown in Equation 2.

$$Sum = \overline{A}\overline{B}Cin + X\overline{Y}\overline{Cin} + \overline{X}Y\overline{Cin} + XYCin \quad (1)$$

$$Sum = (X \oplus Y) \oplus Cin \quad (2)$$

Figure 2 shows the Carryout Karnaugh map.

		<i>BCin</i>			
		00	01	11	10
<i>A</i>	0	0	0	1	0
	1	0	1	1	1

Figure 2: K-map of Cout

The equation given from the K-map in Figure 2 is shown in Equation 3. This is the sum of products equation with the minimal amount of terms.

$$Carryout = XY + \overline{X}YCin + X\overline{Y}Cin \quad (3)$$

Using Equation 2, a circuit diagram was drawn to represent both the Sum and Carryout expression. This circuit diagram is shown in Figure 3, both expressions use the same inputs but go to different outputs represent as Sum and Cout.

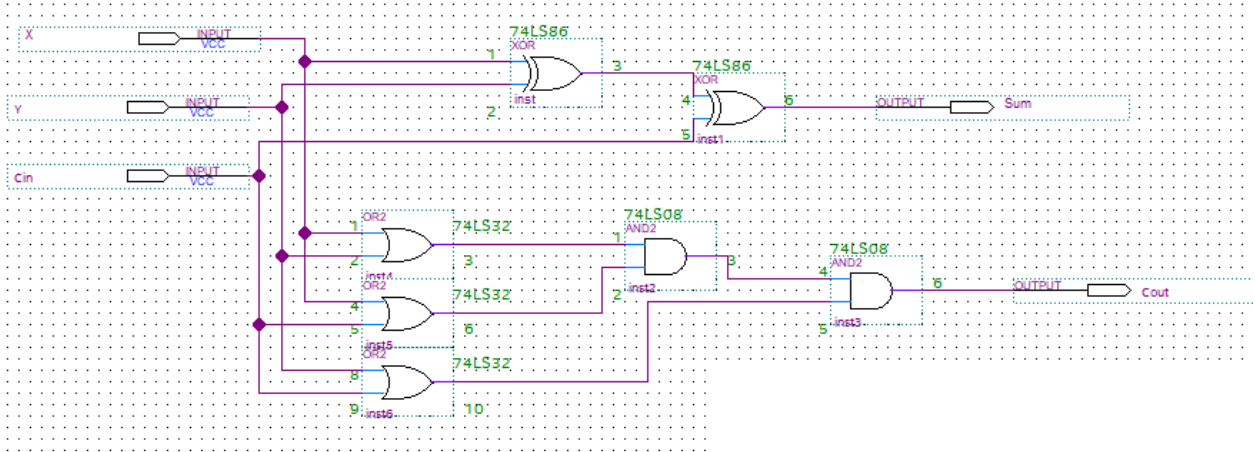


Figure 3: The schematic diagram of the Sum and Cout expressions

A schematic diagram was also designed for the four-bit adder/subtractor shown in Figure 4. The way the adder/subtractor knows whether to add or subtract is by using a control line represented in Figure 4 as Co, which told the chip whether to add or subtract. The four-bit numbers were also represented in twos-complement, where if the number was negative the binary 1s and 0s would be flipped and one would be added to the number, this allowed for negatives to be added and subtracted.

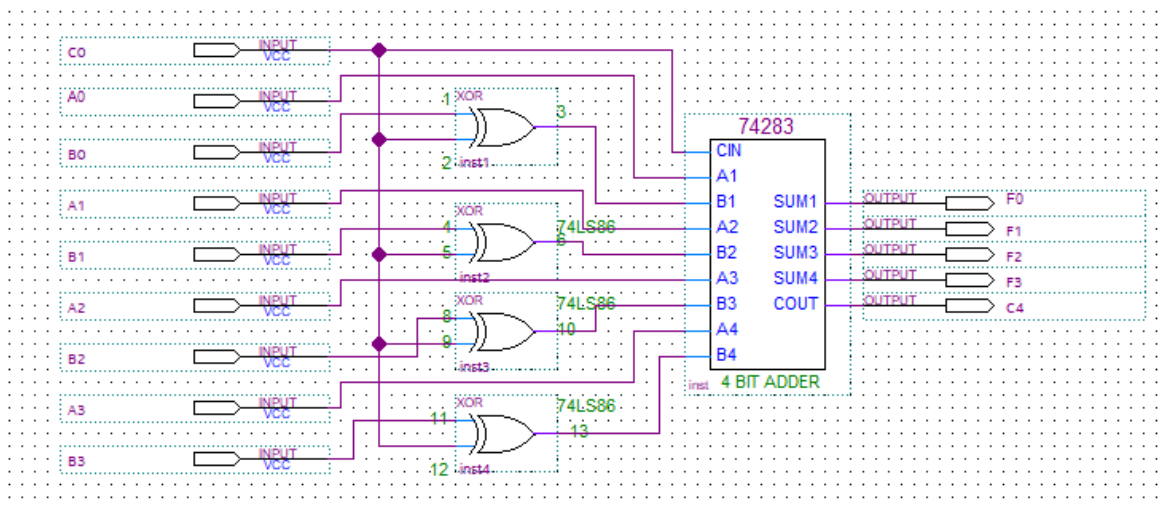


Figure 4: The schematic diagram of the four-bit adder/subtractor

The circuit diagram in Figure 3 was used to simulate the waveform of the equation and compared to a test bench to confirm the correctness of the circuit. The schematic in Figure 3 and Figure 4 were also used to implement the one-bit full adder and four-bit adder/subtractor circuit on the breadboard, to show the correctness of the schematic, and the four-bit adder/subtractor results table.

Results

The waveform in Figure 5 matched the waveform in the test bench exactly and shows the circuit diagram was correct.

 


Figure 5: The ModelSim representation of Sum and Carryout

A table was also given to test the accuracy of the four-bit full adder/subtractor, this tested the subtraction and addition functions by giving two four-bit numbers. Some of the numbers that were given were unable to be represented in the five bits of output that the four-bit full adder/subtractor has and therefore shows the limited capability of the four-bits. Table 1 shows the expected results in decimal and the results that actually occurred in binary.

Table 1: Four-bit addition and subtraction

A3 A2 A1 A0	B3 B2 B1 B0	C4	F3 F2 F1 F0	A + B = F
S7 S6 S5 S4	S3 S2 S1 S0	L4	L3 L2 L1 L0	(Decimal)
0011	0100	0	0111	(3) + (4) = 7
1010	0101	0	1111	(-6) + (5) = -1
1010	0011	0	1101	(-6) + (3) = -3
1111	0110	1	0101	(-1) + (6) = 5
1111	1111	1	1110	(-1) + (-1) = -2
A3 A2 A1 A0	B3 B2 B1 B0	C4	F3 F2 F1 F0	A - B = F
S7 S6 S5 S4	S3 S2 S1 S0	L4	L3 L2 L1 L0	(Decimal)
0111	0011	1	0100	(7) - (3) = 4
1010	0011	1	0111	(-6) - (3) = 7
1111	0110	1	1001	(-1) - (6) = -7
1111	1111	1	0000	(-1) - (-1) = 0
0101	1010	0	1011	(5) - (-6) = -5

Conclusion

The use of K-maps and boolean algebra to create and design binary arithmetic circuits allows for the most efficient version of the circuit to be made. It is important to confirm the simplified equations are equal to expected equation using Modelsim to compare the waveforms of the schematic, as well as use a results table to confirm the correctness of the four-bit full adder/subtractor. The exercise proved successful for both the one-bit full adder and four-bit full adder/subtractor.

Questions

1.

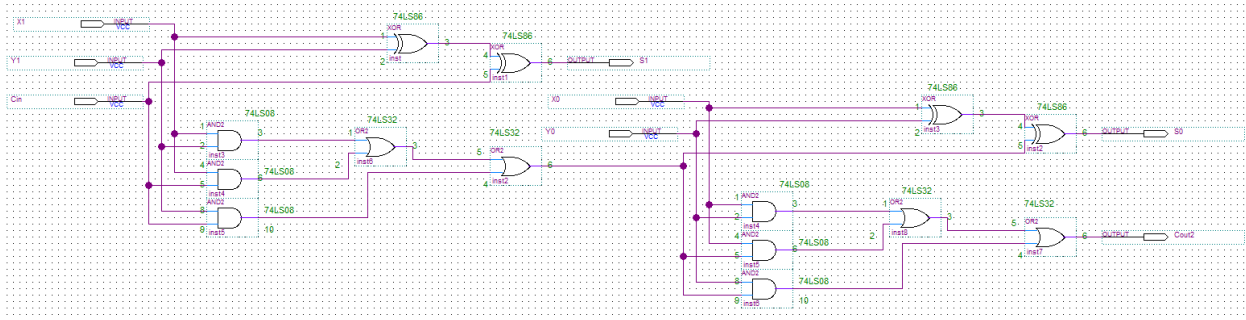


Figure 6: Diagram of a two-bit carry-ripple adder

2. The overflow can be detected if the most significant bit and the carryout of the most significant bit are XORED together as shown in Equation 4.

$$C2 \oplus C3 \quad (4)$$

3. The four bit adder/subtractor produces incorrect two's complement results when there is an overflow because it does not have any way of dealing with numbers outside the range of 7 to -8.

4. No the correct answer would still not be found, the equation $(-1) + (6)$, $(1111 + 0110)$ would return 10101 which is equal to (-11) not (5) , which is the correct answer.

5.

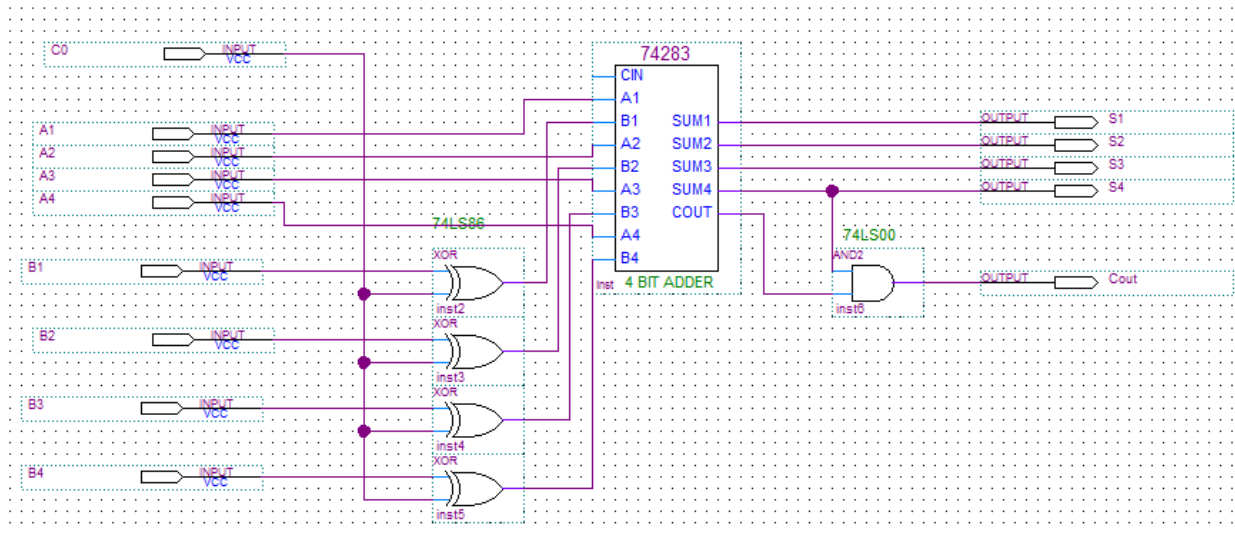


Figure 7: Diagram of a 4-bit adder/subtractor